
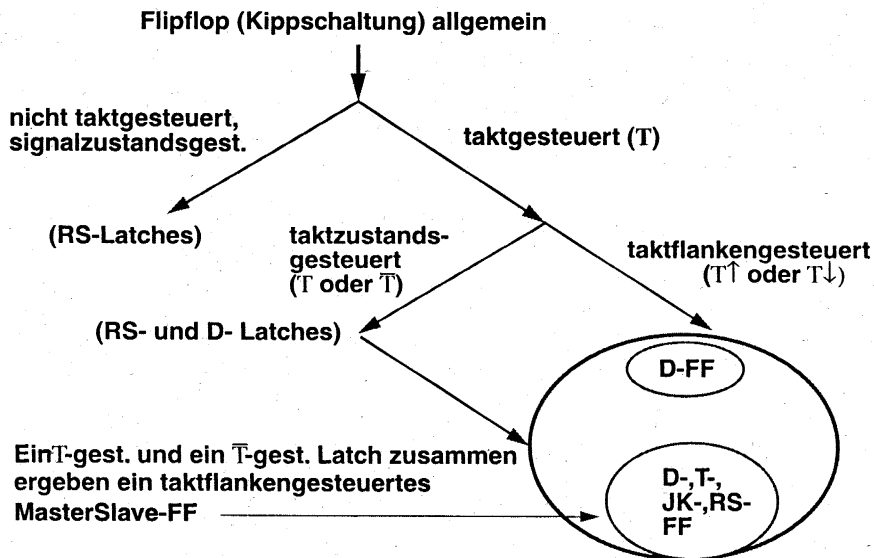


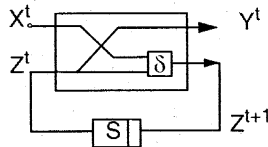
Übersicht über die Flipflop-Arten (Kippschaltungen)





MEDVEDEV - AUTOMAT



MOORE - AUTOMAT

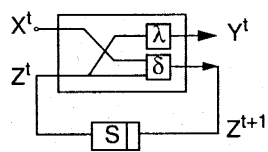

MEALY - AUTOMAT

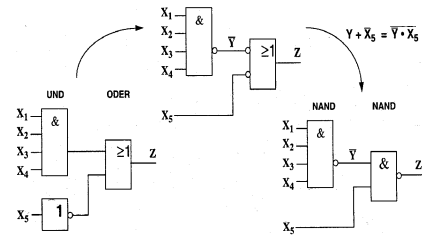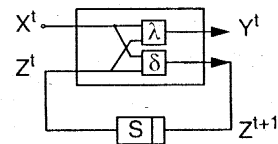

Übergangstabellen

D-FF

Q^t	D	Q^{t+1}
0	0	0
0	1	1
1	0	0
1	1	1

Ansteuertabellen

Q^t	Q^{t+1}	D
0	0	0
0	1	1
1	0	0
1	1	1

T-FF

Q^t	T	Q^{t+1}
0	0	0
0	1	1
1	0	1
1	1	0

Q^t	Q^{t+1}	T
0	0	0
0	1	1
1	0	1
1	1	0

JK-FF

Q^t	J	K	Q^{t+1}
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0

Q^t	Q^{t+1}	J	K
0	0	0	-
0	1	1	-
1	0	-	1
1	1	-	0